

# 3 to 8 Decoder through VAMAN ARM-GCC

Kukunuri Sampath Govardhan

## CONTENTS

<b>I</b>	<b>Components</b>	<b>1</b>
<b>II</b>	<b>Hardware</b>	<b>1</b>
<b>III</b>	<b>Software</b>	<b>1</b>
<b>IV</b>	<b>Solution</b>	<b>1</b>
<b>V</b>	<b>Conclusion</b>	<b>1</b>

**Abstract**—This document shows how to use VAMAN Board as a 3 to 8 Decoder

X	Y	Z
IO_28	IO_29	IO_31

TABLE III

## III. SOFTWARE

**Problem 3.1** Now execute the following program and verify all the outputs as mentioned in Truth table (Table 4) by modifying the inputs X, Y, Z to 0's and 1's respectively.

wget [https://github.com/mygit-sampath-govardhan/fwc-iith-assignments/blob/09f0300f7c4e978e90bd83b2fc8915eab9db8b98/Assignment-9\(ARM-3to8%20decoder\)/codes/src/main.c](https://github.com/mygit-sampath-govardhan/fwc-iith-assignments/blob/09f0300f7c4e978e90bd83b2fc8915eab9db8b98/Assignment-9(ARM-3to8%20decoder)/codes/src/main.c)

## I. COMPONENTS

Component	Value	Qunatity
Resistor	220Ohm	8
LED	Red	8
VAMAN Board		1
Jumper Wires	M-F	20
BreadBoard		1

TABLE I

**Note:** Output pins IO\_4-8,IO\_10-12 are referenced as A-H respectively and input pins IO\_28,29,31 are referred as X,Y,Z respectively.

X	Y	Z	A	B	C	D	E	F	G	H
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

TABLE IV  
TRUTH TABLE

## II. HARDWARE

**Problem 2.1** Make connections between the Vaman Board(PYGMY) and LED's as shown in Table 2

**Problem 2.2** Connect anodes of LED's to the pins using resistors and cathodes to ground(gnd).

IO_4	IO_5	IO_6	IO_7	IO_8	IO_10	IO_11	IO_12
led1	led2	led3	led4	led5	led6	led7	led8

TABLE II

**Problem 2.3** Connect the input pins X, Y, Z to Vaman as shown in Table 3.

## IV. SOLUTION

In the Truth table (Table3) X,Y,Z are inputs and A,B,C,D,E,F,G,H are outputs. This table represents the system that behaves as a 3 to 8 decoder. Using Boolean logic,

$$A = X' Y' Z'$$

$$B = X' Y' Z$$

$$C = X' Y Z'$$

$$D = X' Y Z$$

$$E = X Y' Z'$$

$$F = X Y' Z$$

$$G = X Y Z'$$

$$H = X Y Z$$

#### V. CONCLUSION

A 3 to 8 decoder has 3 inputs and 8 outputs are generated using these 3 inputs.

Here 3 to 8 decoder with Vaman Board has been successfully verified.