

3 to 8 Decoder through Arduino UNO

Kukunuri Sampath Govardhan

CONTENTS

| | | |
|------------|-------------------|---|
| I | Components | 1 |
| II | Hardware | 1 |
| III | Software | 1 |
| IV | Conclusion | 2 |

Abstract—This document shows how to use Arduino UNO as a 3 to 8 Decoder

III. SOFTWARE

Problem 3.1 Now execute the following program and verify all the outputs as mentioned in Truth table (Table 4) by modifying the inputs X, Y, Z to 0's and 1's respectively.

wget <https://github.com/mygit-sampath-govardhan/fwc-iith-assignments/blob/03990e0f3d94cb11d4ac1dd9746aa760653f5f37/Assignment-1/Assignment1-code.cpp>

Note: Output pins d2-d9 are referenced as A-H respectively and input pins d10-d12 are referred as X,Y,Z respectively.

I. COMPONENTS

| Component | Value | Qunatity |
|--------------|--------|----------|
| Resistor | 220Ohm | 8 |
| LED | Red | 8 |
| Arduino | UNO | 1 |
| Jumper Wires | M-M | 20 |
| BreadBoard | | 1 |

TABLE I

II. HARDWARE

Problem 2.1 Make connections between the Arduino UNO and LED's as shown in Table 2

Problem 2.2 Connect anodes of LED's to the pins using resistors and cathodes to ground(gnd).

| | | | | | | | |
|------|------|------|------|------|------|------|------|
| d2 | d3 | d4 | d5 | d6 | d7 | d8 | d9 |
| led1 | led2 | led3 | led4 | led5 | led6 | led7 | led8 |

TABLE II

Problem 2.3 Connect the pins X, Y, Z to arduino as shown in Table 3.

| X | Y | Z |
|-----|-----|-----|
| d10 | d11 | d12 |

TABLE III
TRUTH TABLE

| X | Y | Z | A | B | C | D | E | F | G | H |
|---|---|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

TABLE IV
TRUTH TABLE

Solution : In the Truth table (Table3) X,Y,Z are inputs and A,B,C,D,E,F,G,H are outputs. This table represents the system that behaves as a 3 to 8 decoder. Using Boolean logic,

$$A = X' Y' Z'$$

$$B = X' Y' Z$$

$$C = X' Y Z'$$

$$D = X' Y Z$$

$$E = X Y' Z'$$

$$F = X Y' Z$$

$$G = X Y Z'$$

$$H = X Y Z$$

IV. CONCLUSION

A 3 to 8 decoder has 3 inputs and 8 outputs are generated using these 3 inputs.

Here 3 to 8 decoder has been successfully verified.